

No. of Printed Pages: 2

Roll No.

3rd sem./ECE

Subject: Network Filter and Transmission Line

Time: 3 Hrs.

M.M. :100

SECTION – A

Note: Very Short Answer type question. Attempt any 10 Parts.

(10*2=20)

Q.1 Answer the following question briefly: -

- a) Define Asymmetrical network?
- b) Differentiate Balanced and Unbalanced Network using circuit diagram?
- c) What is image impedance?
- d) Explain 'Decibel' and 'Neper' with suitable mathematical expression?
- e) Write down the Expression for the symmetrical T Type Attenuator?
- f) Define Cut-off frequency in Filters?
- g) What are Primary Constant and Secondary Constant in Transmission Line?
- h) Define VSWR?
- i) Define Reflection Coefficient?
- j) What is stub matching?
- k) Define Characteristic Impedance?
- l) Define Broadband matching?
- m) What is the Disadvantage of Constant K-type filter over M-derived filter?
- n) Define infinite frequency in M-derived filter?

SECTION -B

Note: Short Answer Type Questions. Attempt any Five parts

(5*4=20)

- Q.2
- i) Derive the relationship between Characteristic Impedance of symmetrical T and π Network?
 - ii) Explain Image Transfer Constant?
 - iii) Write a short note on Crystal Filter?

- iv) Establish the relation between cut off frequency and infinite frequency of attenuation for m-derived low pass filter?
- v) Derive the expression for Distortion less transmission line?
- vi) Write a note on iterative impedance of Asymmetrical T network?
- vii) Write down the complete analysis of the composite filter?
- viii) A transmission line has the following primary co-efficient at frequency 5 KHz.
 $R=30 \text{ ohm/km}$ $L=1.5 \text{ mH/km}$ $G=2 \text{ uMho/km}$ $C=0.5 \text{ uF/km}$
 Calculate Characteristic Impedance and Attenuation Constant?

SECTION- C

Note: Long Answer Type Questions. Attempt any Three question (3*20=60)

- Q.3 a) Derive the Expression for Propagation constant for symmetrical π Network?
 b) Write a note on Various Network Configuration?
- Q.4 a) Design the various design parameters of symmetrical ' π ' type attenuator?
 b) Also Find the design impedance (R_0) and attenuator per section of a symmetrical ' π ' type attenuator having series arm of 275 ohm and shunt arm each of 450 ohm.
- Q.5 a) Derive the characteristic impedance of constant k-type high pass filter?
 b) Differentiate between Active and Passive Filter?
- Q.6 a) Derive the expression for gain of Butterworth low pass filter?
 b) Write a short note on complete classification of filters?
- Q.7 a) Explain Quarter wave transformer?
 b) Write down the various advantages of stub matching in Transmission Line?